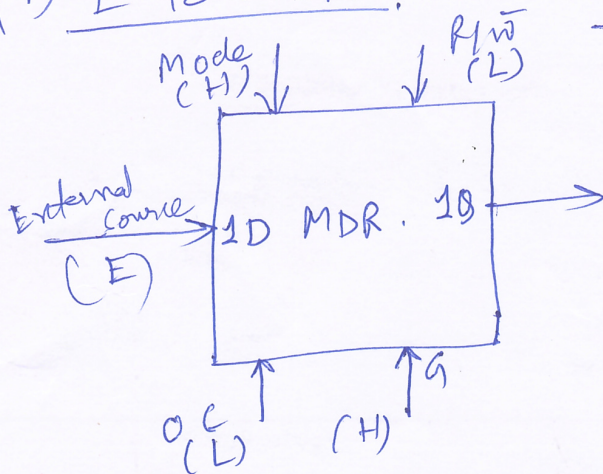


Experiment no 3

(1) E to MDR




Mode	R/W	E	G	OC	Q	Remarks
1	0	0	1	0	0	Read 0 from E and write in MDR
1	0	1	1	0	1	Read 1 from E and write in MDR

Function table (74373)

Mode	R/W	E	Event
0	1	—	Read MDR
1	1	—	—
0	0	—	Write from RAM to MDR
1	0	—	Write from E to MDR

(2) MDR to RAM

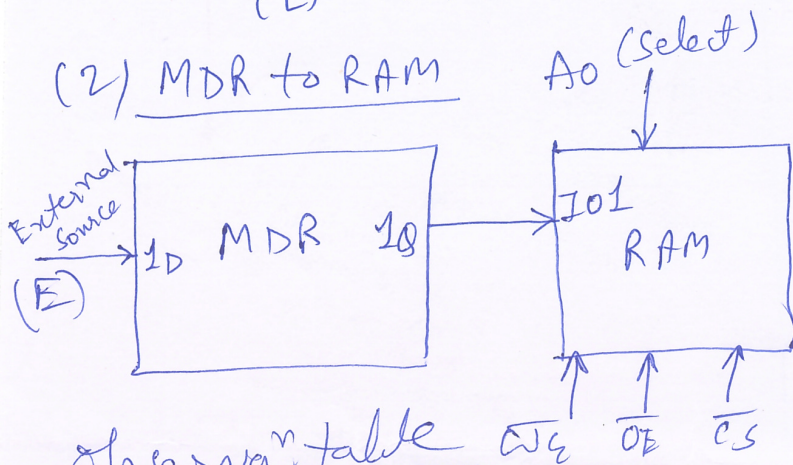


Op Control (OC)	G	D	Q	Event
L	H	H	HZ	Write
L	H	L	L	—
L	L	X	Q0	Read
H	X	X	HIZ	High impedance

Observation table

Mode	R/W	OC	G	WE	CS	OE	E	Q	A0	Z01	Remarks
											Read 0 from MDR
											Write in RAM from MDR
											Read 1 from MDR
											Write 1 in RAM from MDR

(3) RAM to MDR

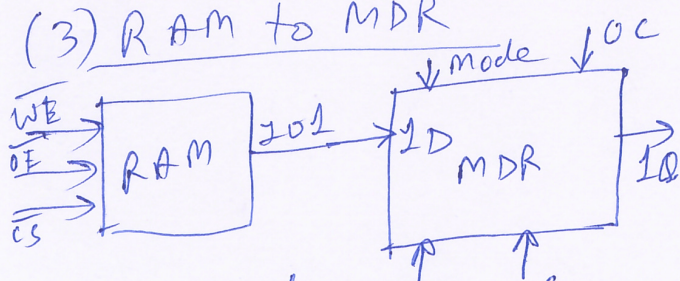

Mode	R/W	OC	G	WE	CS	OE	A0	Z01	ID	IO	Remarks
											Read 0 from RAM & write in MDR
											Read 1 from RAM & write in MDR